
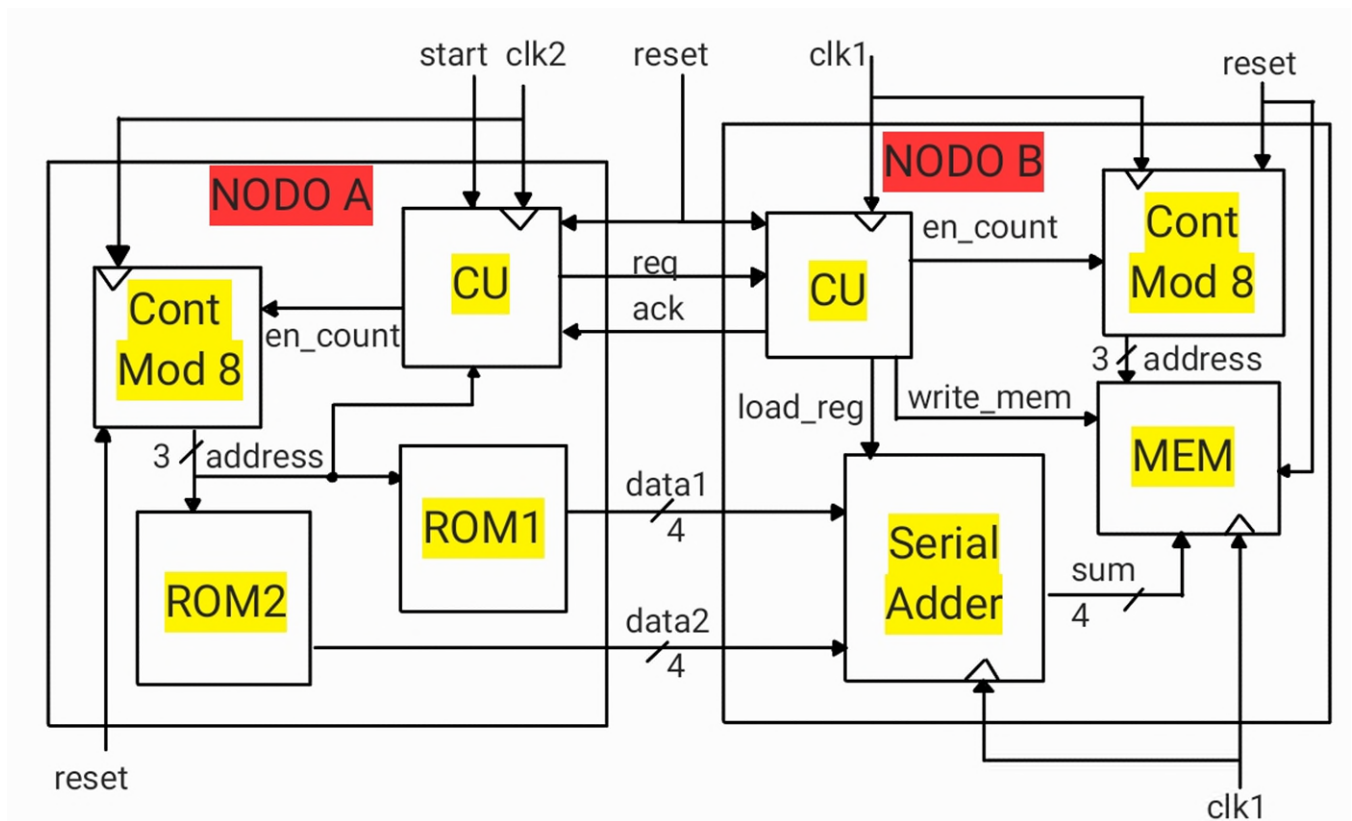



Progettare, implementare in VHDL e simulare la seguente architettura. Un sistema è composto da due nodi, A e B. A contiene 2 ROM, ROM1 e ROM2, in cui sono memorizzate 8 stringhe da 4 bit ciascuno. A legge una stringa da ROM1 e una stringa da ROM2 e le invia, una alla volta mediante handshaking semplice, a B. B somma le 2 stringhe ricevute utilizzando un sommatore seriale (cioè, un sommatore che calcola la somma un bit alla volta iterativamente) e memorizza il risultato in una memoria interna MEM.

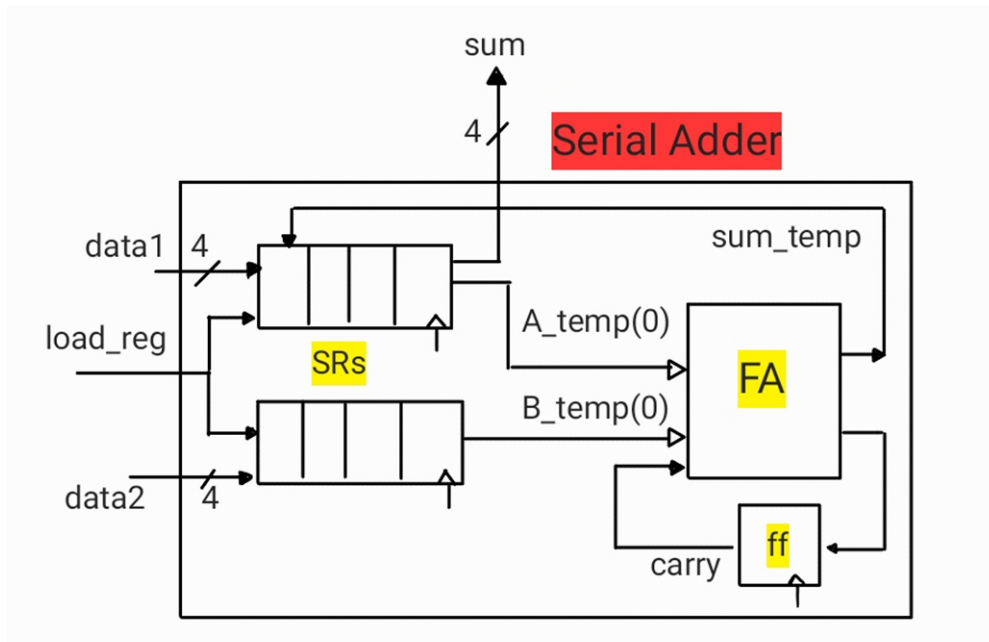Nota: seppure sia possibile implementare la funzione dei singoli moduli come le memorie o i registri con paradigma, ad esempio, data-flow o comportamentale, è richiesto che l'implementazione VHDL segua una progettazione strutturale per l'interconnessione dei moduli.






- Diagramma degli stati di A

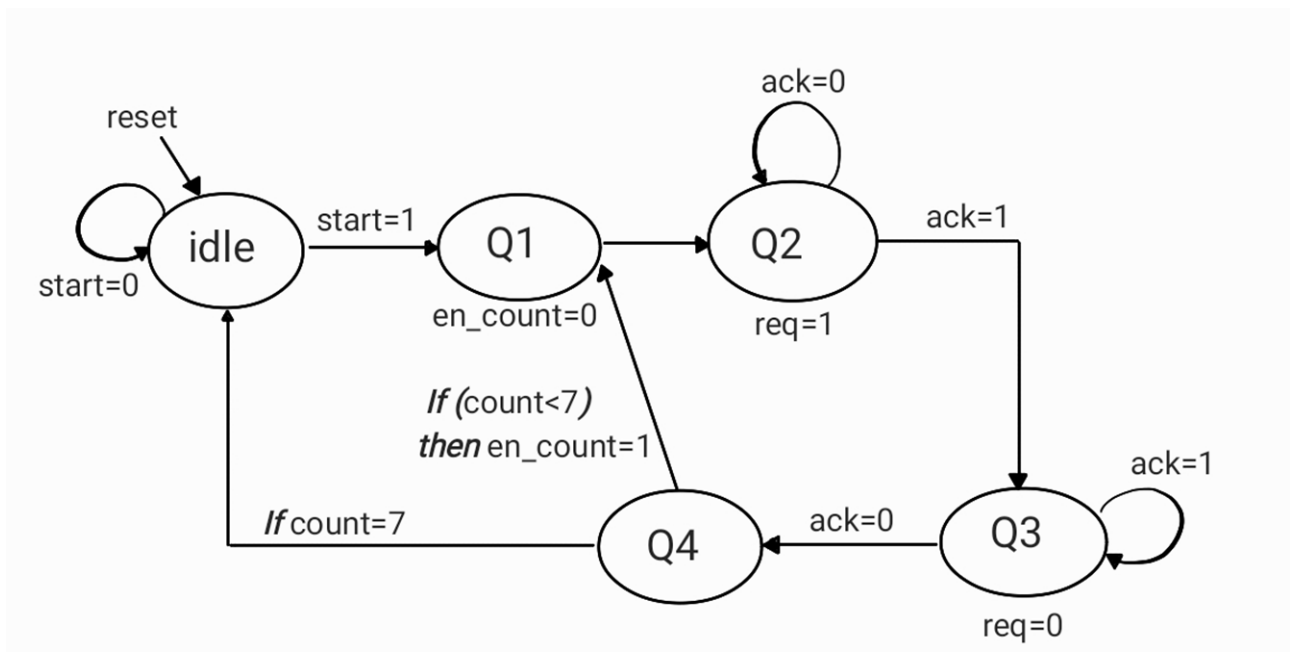

- Diagramma degli stati di B

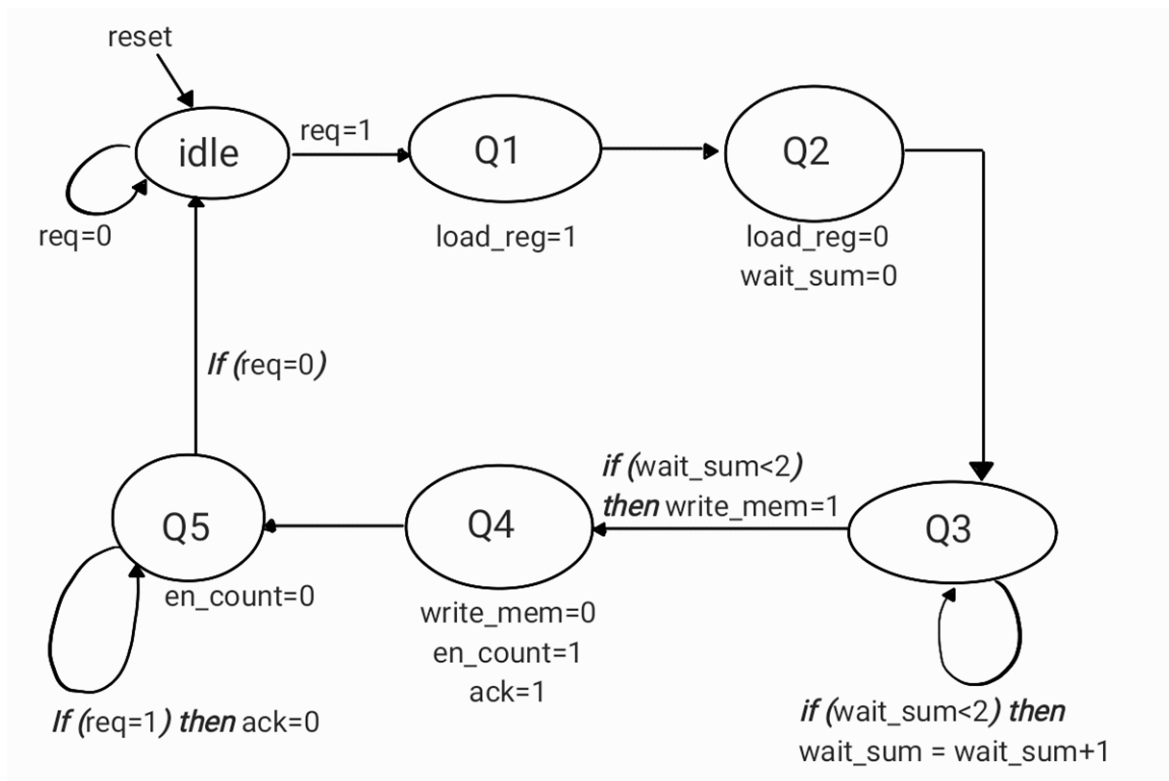

NODO A

ROM1.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;

entity ROM1 is
    generic (
        DATA_WIDTH      : integer := 8;    -- Larghezza del dato in bit
        DEPTH              : integer := 16;   -- Dimensione della ROM
        ADDRESS_WIDTH     : integer := 4     -- Larghezza dell'indirizzo in bit
    );
    Port (
        address : in  STD_LOGIC_VECTOR(ADDRESS_WIDTH-1 downto 0);
        dataOut  : out STD_LOGIC_VECTOR(DATA_WIDTH-1 downto 0)
    );
end ROM1;

architecture Behavioral of ROM1 is

    type ROMArray is array (0 to DEPTH-1) of STD_LOGIC_VECTOR(DATA_WIDTH-1
downto 0);
    signal rom_data : ROMArray;

```

```

begin

    init_ROM: process -- 0,1,2,3,4...,DEPTH-2,DEPTH-1
    begin
        for i in 0 to DEPTH-1 loop
            rom_data(i) <= std_logic_vector(to_unsigned(i,DATA_WIDTH));
        end loop;
        wait;
    end process;

    process(address)
    begin
        dataOut <= rom_data(to_integer(unsigned(address)));
    end process;
end Behavioral;

```

ROM2.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;

entity ROM2 is
    generic (
        DATA_WIDTH      : integer := 8;    -- Larghezza del dato in bit
        DEPTH             : integer := 16;   -- Dimensione della ROM
        ADDRESS_WIDTH     : integer := 4     -- Larghezza dell'indirizzo in bit
    );
    Port (
        address : in STD_LOGIC_VECTOR(ADDRESS_WIDTH-1 downto 0);
        dataOut : out STD_LOGIC_VECTOR(DATA_WIDTH-1 downto 0)
    );
end ROM2;

architecture Behavioral of ROM2 is

    type ROMArray is array (0 to DEPTH-1) of STD_LOGIC_VECTOR(DATA_WIDTH-1
downto 0);
    signal rom_data : ROMArray;

begin

    init_ROM: process -- DEPTH-1,DEPTH-2,DEPTH-3,...,1,0
    begin
        for i in 0 to DEPTH-1 loop
            rom_data(i) <= std_logic_vector(to_unsigned(DEPTH-1-i, DATA_WIDTH));
        end loop;
        wait;
    end process;

```

```

    end process;

    process(address)
    begin
        dataOut <= rom_data(to_integer(unsigned(address)));
    end process;
end Behavioral;

```

counter.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity counter is
    generic (
        WIDTH : integer := 8 -- Numero di bit usati per rappresentare il
conteggio
    );
    Port (
        clk      : in STD_LOGIC;
        rst      : in STD_LOGIC;
        enable   : in STD_LOGIC;
        count    : out STD_LOGIC_VECTOR(WIDTH-1 downto 0)
    );
end counter;

architecture Behavioral of counter is

    signal c : STD_LOGIC_VECTOR(WIDTH-1 downto 0) := (others => '0');

begin
    process(clk, rst)
    begin
        if rst = '1' then
            c <= (others => '0');
        elsif rising_edge(clk) and enable = '1' then
            c <= c + 1;
        end if;
    end process;

    count <= c;
end Behavioral;

```

control_unit_A.vhd

```

library IEEE;

```

```

use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

entity control_unit_A is
    Port ( clock : in STD_LOGIC;
          start : in STD_LOGIC;
          reset : in STD_LOGIC;
          ack : in std_logic;
          req : out std_logic;
          address : in std_logic_vector(2 downto 0);
          enable_cont : out std_logic
        );
end control_unit_A;

architecture Behavioral of control_unit_A is

    type stato is (idle, Q1, Q2, Q3, Q4);
    signal stato_corrente : stato := idle;

begin

process(clock)
    begin
        if rising_edge(clock) then
            if reset = '1' then
                stato_corrente <= idle;
            else
                case stato_corrente is
                    when idle =>
                        if(start='1') then
                            stato_corrente <= Q1;
                        else
                            stato_corrente <= idle;
                        end if;

                    when Q1 =>
                        enable_cont <= '0';
                        stato_corrente <= Q2;

                    when Q2 =>
                        req <= '1';
                        if(ack='0') then
                            stato_corrente <= Q2;
                        else stato_corrente <= Q3;
                        end if;

                    when Q3 =>
                        req <= '0';
                        if(ack='1') then
                            stato_corrente <= Q3;

```

```

        else
            stato_corrente <= Q4;
        end if;

        when Q4 =>
            if(address="111") then
                stato_corrente <= idle;
            else
                enable_cont <= '1';
                stato_corrente <= Q1;
            end if;
        end case;
    end if;
end if;
end process;

end Behavioral;

```

node_A.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity node_A is
    Port ( clock : in STD_LOGIC;
          start : in STD_LOGIC;
          reset : in STD_LOGIC;
          ack : in std_logic;
          req : out std_logic;
          data1 : out std_logic_vector(3 downto 0);
          data2 : out std_logic_vector(3 downto 0) );
end node_A;

architecture Behavioral of node_A is
    component ROM1 is
        generic (
            DATA_WIDTH      : integer := 8;
            DEPTH             : integer := 16;
            ADDRESS_WIDTH    : integer := 4
        );
        Port (
            address : in STD_LOGIC_VECTOR(ADDRESS_WIDTH-1 downto 0);
            dataOut : out STD_LOGIC_VECTOR(DATA_WIDTH-1 downto 0)
        );
    end component;

    component ROM2 is
        generic (
            DATA_WIDTH      : integer := 8;

```

```

        DEPTH          : integer := 16;
        ADDRESS_WIDTH : integer := 4
    );
    Port (
        address : in STD_LOGIC_VECTOR(ADDRESS_WIDTH-1 downto 0);
        dataOut : out STD_LOGIC_VECTOR(DATA_WIDTH-1 downto 0)
    );
end component;

component counter is
    generic (
        WIDTH : integer := 8
    );
    Port (
        clk      : in STD_LOGIC;
        rst      : in STD_LOGIC;
        enable   : in STD_LOGIC;
        count    : out STD_LOGIC_VECTOR(WIDTH-1 downto 0)
    );
end component;

component control_unit_A is
    Port ( clock : in STD_LOGIC;
           start : in STD_LOGIC;
           reset : in STD_LOGIC;
           ack   : in std_logic;
           req   : out std_logic;
           address : in std_logic_vector(2 downto 0);
           enable_cont : out std_logic
    );
end component;

signal address : std_logic_vector(2 downto 0);
signal enable_count : std_logic;
begin
    cont_addr: counter
        generic map (
            WIDTH => 3
        )
        port map(
            clk => clock,
            rst => reset,
            enable => enable_count,
            count => address
        );

    mem1 : ROM1
        generic map (
            DATA_WIDTH => 4,
            DEPTH => 8,

```



```

        ADDRESS_WIDTH => 3
    ) port map (
        address => address,
        dataOut => data1
    );

mem2 : ROM2
    generic map (
        DATA_WIDTH => 4,
        DEPTH => 8,
        ADDRESS_WIDTH => 3
    ) port map (
        address => address,
        dataOut => data2
    );

cu_A : control_unit_A
    port map (
        clock => clock,
        start => start,
        reset => reset,
        ack => ack,
        req => req,
        address => address,
        enable_cont => enable_count
    );

end Behavioral;

```

node_A_tb.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity nodo_A_tb is
end nodo_A_tb;

architecture behavior of nodo_A_tb is
    signal tb_clock : std_logic := '0';
    signal tb_start : std_logic := '0';
    signal tb_reset : std_logic := '0';
    signal tb_ack : std_logic := '0';
    signal tb_req : std_logic;
    signal tb_data1 : std_logic_vector(3 downto 0);
    signal tb_data2 : std_logic_vector(3 downto 0);

    constant clk_period : time := 10 ns;

    component node_A is

```

```

    Port (
        clock : in STD_LOGIC;
        start  : in STD_LOGIC;
        reset  : in STD_LOGIC;
        ack    : in std_logic;
        req    : out std_logic;
        data1  : out std_logic_vector(3 downto 0);
        data2  : out std_logic_vector(3 downto 0)
    );
end component;

begin
    uut: node_A port map (
        clock => tb_clock,
        start  => tb_start,
        reset  => tb_reset,
        ack    => tb_ack,
        req    => tb_req,
        data1  => tb_data1,
        data2  => tb_data2
    );

    clk : process
    begin
        tb_clock <= '0';
        wait for clk_period / 2;
        tb_clock <= '1';
        wait for clk_period / 2;
    end process;


    stim: process
    begin
        wait for 10 ns;

        tb_start <= '1';
        wait for 10 ns;
        tb_start <= '0';

        for i in 1 to 8 loop
            wait for 30 ns;
            tb_ack <= '1';
            wait for 10 ns;
            tb_ack <= '0';
        end loop;

        wait;
    end process;
end behavior;

```

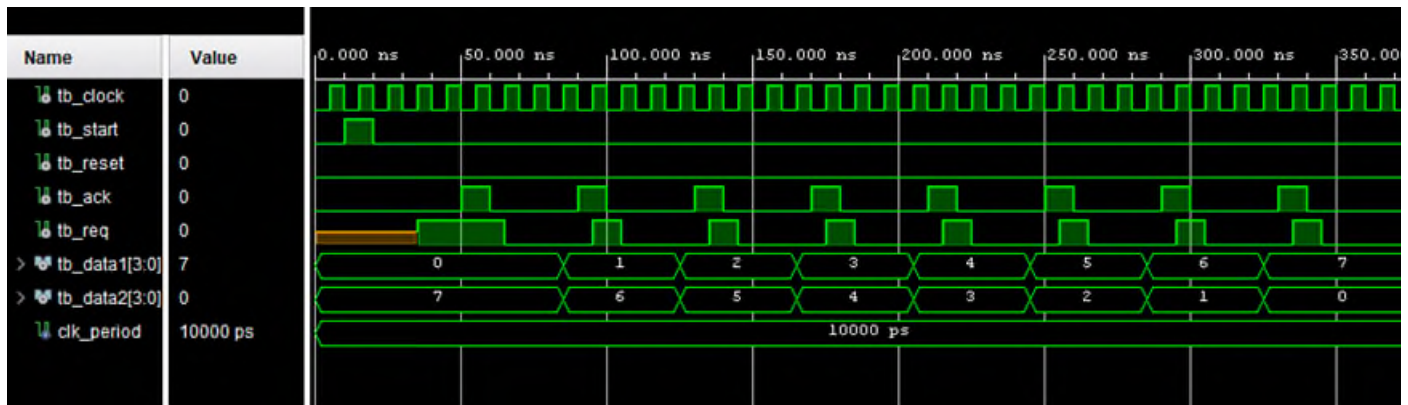

NODO B

MEM.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity memory is
    generic (
        DATA_WIDTH : integer := 8;    -- Larghezza del dato in bit
        DEPTH        : integer := 16;   -- Dimensione della memoria
        ADDR_WIDTH   : integer := 4     -- Larghezza dell'indirizzo in bit
    );
    Port (
        clk      : in STD_LOGIC;
        rst      : in STD_LOGIC;
        write     : in STD_LOGIC;
        read      : in STD_LOGIC;
        address   : in STD_LOGIC_VECTOR(ADDR_WIDTH-1 downto 0);
        dataIn    : in STD_LOGIC_VECTOR(DATA_WIDTH-1 downto 0);
        dataOut   : out STD_LOGIC_VECTOR(DATA_WIDTH-1 downto 0)
    );
end memory;

architecture Behavioral of memory is

    type array_memoria is array (0 to DEPTH-1) of STD_LOGIC_VECTOR(DATA_WIDTH-1
downto 0);
    signal memoria_interna : array_memoria := (others => (others => '0'));

begin
    process(clk, rst)
    begin
        if rst = '1' then

```

```

        memoria_interna <= (others => (others => '0'));

    elsif rising_edge(clk) then

        if write = '1' then
            memoria_interna(to_integer(unsigned(address))) <= dataIn;
        end if;

        if read = '1' then
            dataOut <= memoria_interna(to_integer(unsigned(address)));
        end if;

    end if;
end process;
end Behavioral;

```

serial_adder.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity serial_adder is
    generic (
        N : INTEGER := 4
    );
    port(
        clock : in STD_LOGIC;
        A : in STD_LOGIC_VECTOR (N-1 downto 0);
        B : in STD_LOGIC_VECTOR (N-1 downto 0);
        load : in STD_LOGIC;
        sum : out STD_LOGIC_VECTOR(N-1 downto 0)
    );
end serial_adder;

architecture Behavioral of serial_adder is

    signal carry: STD_LOGIC;
    signal A_temp: STD_LOGIC_VECTOR(N-1 downto 0);
    signal B_temp: STD_LOGIC_VECTOR(N-1 downto 0);

begin

    process(clock)
        variable sum_temp: STD_LOGIC;
    begin
        if(rising_edge(clock)) then
            if (load = '1') then
                A_temp <= A;
            end if;
        end if;
    end process;

```

```

        B_temp <= B;
        carry <= '0';
        end if;
    else
        B_temp <= (B_temp(0) & B_temp(N-1 downto 1));
        sum_temp := (A_temp(0) xor B_temp(0)) xor (carry);
        A_temp <= (sum_temp & A_temp(N-1 downto 1));
        carry <= (((A_temp(0) xor B_temp(0)) and carry)) or
(A_temp(0) and B_temp(0));
        end if;
    end process;

    sum <= A_temp;

end Behavioral;

```

serial_adder_tb.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.STD_LOGIC_TEXTIO.ALL;
use STD.TEXTIO.ALL;

entity serial_adder_tb is
end serial_adder_tb;

architecture testbench of serial_adder_tb is

    component serial_adder
        port (
            A : in std_logic_vector (3 downto 0);
            B : in std_logic_vector (3 downto 0);
            clock : in std_logic;
            load : in std_logic;
            sum : out std_logic_vector (3 downto 0)
        );
    end component;

    signal A : std_logic_vector (3 DownTo 0) := "0000";
    signal B : std_logic_vector (3 DownTo 0) := "0000";
    signal clock : std_logic := '0';
    signal load : std_logic := '0';
    signal sum : std_logic_vector (3 downto 0) := "0000";

begin
    dut : serial_adder
        port map (

```

```


        A => A,
        B => B,
        clock => clock,
        load => load,
        sum => sum
    );

    clk: process
    begin
        clock <= '0';
        wait for 10ns;
        clock <= '1';
        wait for 10ns;
    end process;

    stim: process
    begin
        wait for 10 ns;
        load <= '1';
        A <= "0010";
        B <= "0001";
        wait for 10 ns;
        load <= '0';

        wait;
    end process;
end testbench;

```

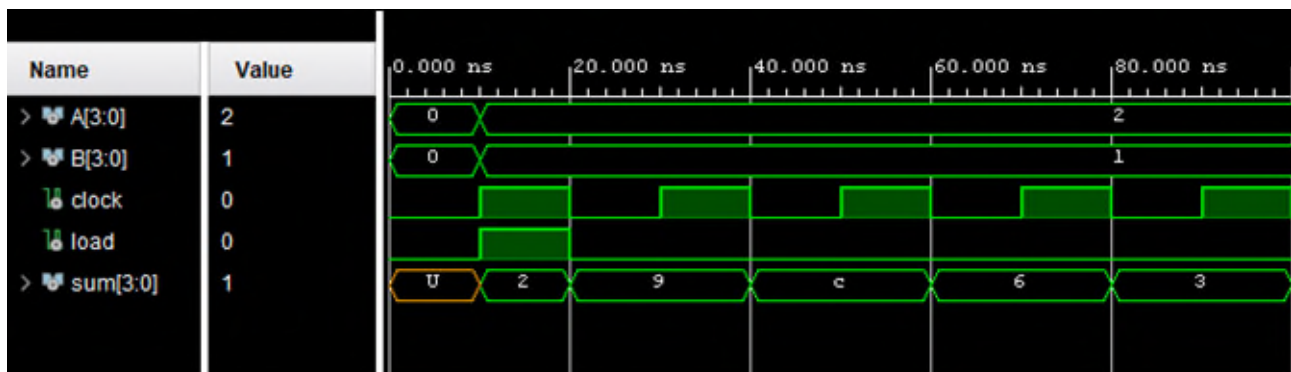

control_unit_B.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

entity control_unit_B is
    Port ( clock : in STD_LOGIC;
          reset : in STD_LOGIC;
          en_count : out STD_LOGIC;

```

```

        load_reg : out STD_LOGIC;
        write_mem : out STD_LOGIC;
        req : in std_logic;
        ack : out std_logic);
end control_unit_B;

architecture Behavioral of control_unit_B is

    type state is (idle, Q1, Q2, Q3, Q4, Q5);
    signal current_state: state;

begin

    process(clock)
        variable wait_sum : integer := 0;
    begin
        if rising_edge(clock) then
            if reset = '1' then
                current_state <= idle;
            else
                case current_state is
                    when idle =>
                        load_reg <= '0';
                        if req = '1' then
                            current_state <= Q1;
                        else
                            current_state <= idle;
                        end if;
                    when Q1 =>
                        load_reg <= '1';
                        en_count <= '0';
                        current_state <= Q2;
                    when Q2 =>
                        load_reg <= '0';
                        wait_sum := 0;
                        current_state <= Q3;
                    when Q3 =>
                        if(wait_sum=2) then
                            write_mem <='1';
                            current_state <= Q4;
                        else
                            wait_sum := wait_sum +1;
                            current_state <= Q3;
                        end if;
                    when Q4 =>
                        write_mem <= '0';

```

```

        en_count <= '1';
        ack <= '1';
        current_state <= Q5;

    when Q5 =>
        en_count <= '0';
        if req = '1' then
            ack <= '0';
            current_state <= idle;
        else
            current_state <= Q5;
        end if;
    end case;
end if;
end if;
end process;

end Behavioral;

```

node_B.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

entity nodo_B is
    Port (
        clock : in std_logic;
        reset : in std_logic;
        req : in std_logic;
        ack : out std_logic;
        data1 : in std_logic_vector(3 downto 0);
        data2 : in std_logic_vector(3 downto 0));
end nodo_B;

architecture Structural of nodo_B is

    component serial_adder is
        generic (N : INTEGER:=4);
        port(
            A: in STD_LOGIC_VECTOR (N-1 downto 0);
            B: in STD_LOGIC_VECTOR (N-1 downto 0);
            clock: in STD_LOGIC;
            load: in STD_LOGIC;
            sum: out STD_LOGIC_VECTOR(N-1 downto 0));
    end component;

    component MEM is
        generic (

```



```

    DATA_WIDTH : integer := 8;
    DEPTH        : integer := 16;
    ADDR_WIDTH   : integer := 4
);
Port (
    clk      : in STD_LOGIC;
    rst      : in STD_LOGIC;
    write     : in STD_LOGIC;
    read      : in STD_LOGIC;
    address   : in STD_LOGIC_VECTOR(ADDR_WIDTH-1 downto 0);
    dataIn    : in STD_LOGIC_VECTOR(DATA_WIDTH-1 downto 0);
    dataOut   : out STD_LOGIC_VECTOR(DATA_WIDTH-1 downto 0)
);
end component;

```

```

component counter is
    generic (
        WIDTH : integer := 8
    );
    Port (
        clk    : in STD_LOGIC;
        rst    : in STD_LOGIC;
        enable  : in STD_LOGIC;
        count   : out STD_LOGIC_VECTOR(WIDTH-1 downto 0)
    );
end component;

```

```

component control_unit_B is
Port ( clock : in STD_LOGIC;
        reset : in STD_LOGIC;
        en_count : out STD_LOGIC;
        load_reg : out STD_LOGIC;
        write_mem : out STD_LOGIC;
        req : in std_logic;
        ack : out std_logic);
end component;

```

```

signal load_reg, write_mem, en_count : std_logic;
signal op1, op2, ris : std_logic_vector(3 downto 0);
signal address : std_logic_vector(2 downto 0);

```

```

begin

```

```

    count: counter
        generic map(
            WIDTH=>3
        ) port map(
            clk => clock,
            rst => reset,
            enable => en_count,

```

```

        count => address
    );

    ser_add : serial_adder
        generic map(
            N=>4
        ) port map(
            A => data1,
            B => data2,
            clock => clock,
            load => load_reg,
            sum => ris);

    m_e_m : MEM
        generic map (
            DATA_WIDTH => 4,
            DEPTH => 8,
            ADDR_WIDTH => 3
        ) port map (
            clk => clock,
            rst => reset,
            write => write_mem,
            read => '0',
            address => address,
            dataIn => ris,
            dataOut => open);

    cu_B : control_unit_B port map (
        clock => clock,
        reset => reset,
        en_count => en_count,
        load_reg => load_reg,
        write_mem => write_mem,
        req => req,
        ack => ack
    );
end Structural;

```

SISTEMA FORMATO DAI NODI A E B

total_system_tb.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity total_system_tb is

```

```

end total_system_tb;

architecture Behavioral of total_system_tb is
    component node_A is
        Port ( clock : in STD_LOGIC;
              start : in STD_LOGIC;
              reset : in STD_LOGIC;
              ack : in std_logic;
              req : out std_logic;
              data1 : out std_logic_vector(3 downto 0);
              data2 : out std_logic_vector(3 downto 0) );
    end component;

    component node_B is
        Port (
            clock : in std_logic;
            reset : in std_logic;
            req : in std_logic;
            ack : out std_logic;
            data1 : in std_logic_vector(3 downto 0);
            data2 : in std_logic_vector(3 downto 0));
    end component;

    signal clk1, clk2, start, rst, ack, req : std_logic := '0';
    signal data1, data2 : std_logic_vector(3 downto 0) := (others=>'0');
begin
    n_A : node_A port map (
        clock => clk2,
        start => start,
        reset => rst,
        ack => ack,
        req => req,
        data1 => data1,
        data2 => data2
    );

    n_B : node_B port map (
        clock => clk1,
        reset => rst,
        ack => ack,
        req => req,
        data1 => data1,
        data2 => data2
    );

    clock_gen1: process
    begin
        wait for 2 ns;
        clk1 <= not clk1;
    end process;

```


```

        clock_gen2: process
begin
    wait for 5 ns;
    clk2 <= not clk2;
end process;

process
begin
    wait for 1 ns;
    start<='1';
    wait for 6 ns;
    start<='0';
    wait for 900 ns;
    wait;
end process;

end Behavioral;

```

 

Name	Design Unit	Name	Value
total_system_tb	total_system_tb(Beha	clk	0
n_A	node_A(Behavioral)	rst	0
n_B	node_B(Structural)	write	0
count	counter(Behavioral)	read	0
ser_add	serial_adder(Behavio	address[2:0]	0
m_e_m	MEM(Behavioral)	dataIn[3:0]	b
cu_B	control_unit_B(Behav	dataOut[3:0]	U
		memoria_interna[0:7][3:0]	7,7,7,7,7,7,7,7
		DATA_WIDTH	4
		DEPTH	8
		ADDR_WIDTH	3